
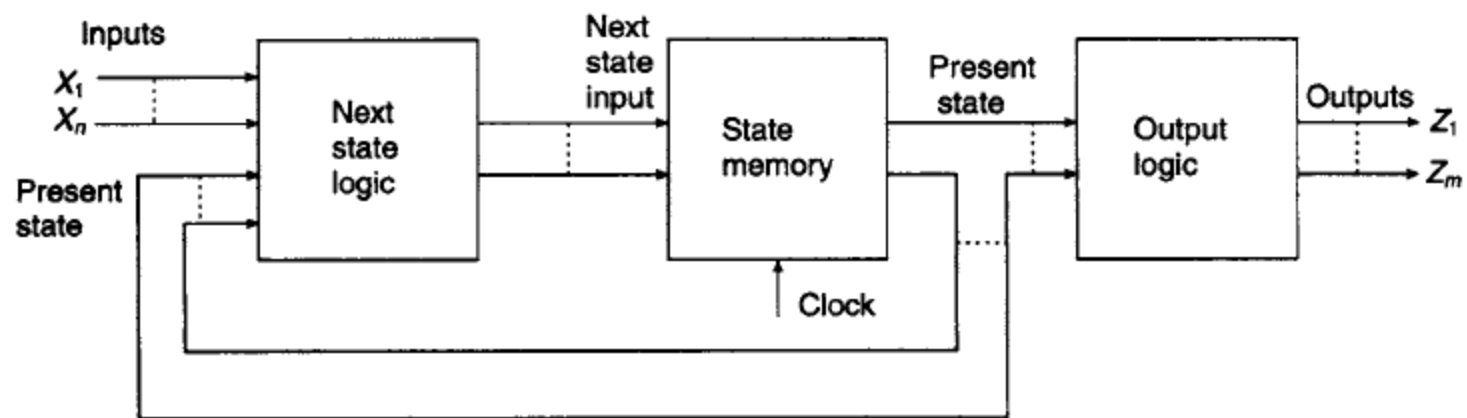

 
# **Finite-State Machines (FSMs) and Controllers**



(a)




(b)

# FSM State Encoding

- Binary encoding: i.e., for four states, 00, 01, 10, 11
- One-hot encoding
  - One state bit per state
  - Only one state bit is HIGH at once
  - I.e., for four states, 0001, 0010, 0100, 1000
  - Requires more flip-flops
  - Often next state and output logic is simpler

# Vending machine block diagram

 


5p=F

10p=T

- Three 5p coins in sequence: F,F,F
- Two 5p coins followed by a 10p: F,F,T
- A 5p coin followed by a 10p: F,T
- A 10p coin followed by a 5p: T,F
- Two 10p coins in sequence: T,T


# State diagram

 

5p=F

10p=T

# Minimized state diagram

 

5p=F  
10p=T

# Minimized transition table

Present state	Inputs		Next state	Output Open
	T	F		
0p	0	0	0p	0
	0	1	5p	0
	1	0	10p	0
	1	1	X	X
5p	0	0	5p	0
	0	1	10p	0
	1	0	15p	0
	1	1	X	X
10p	0	0	10p	0
	0	1	15p	0
	1	0	15p	0
	1	1	X	X
15p	X	X	15p	1

5p=F

10p=T

# Encoded transition table

Present state		Inputs		Next state		Output Open
		T	F	D <sub>1</sub>	D <sub>0</sub>	
Q <sub>1</sub>	Q <sub>0</sub>					
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	X	X	X
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
		1	1	X	X	X
1	0	0	0	1	0	0
		0	1	1	1	0
		1	0	1	1	0
		1	1	X	X	X
1	1	0	0	1	1	1
		0	1	1	1	1
		1	0	1	1	1
		1	1	X	X	X




5p=F

10p=T



# Vending Machine K Maps for D flip flops implementation

## Design Example (Continued)

   

$D_1 = ?$   
 $D_0 = ?$   
Open = ?

# Vending Machine- K Maps for D flip flops implementation

## Design Example (Continued)

Q1Q0		Q1			
		00	01	11	10
TF	00	0	0	1	1
	01	0	1	1	1
T	11	X	X	X	X
	10	1	1	1	1

K-map for  $D_1$

Q1Q0		Q1			
		00	01	11	10
TF	00	0	1	1	0
	01	1	0	1	1
T	11	X	X	X	X
	10	0	1	1	1

K-map for  $D_0$

Q1Q0		Q1			
		00	01	11	10
TF	00	0	0	1	0
	01	0	0	1	0
T	11	X	X	X	X
	10	0	0	1	0


K-map for Open

$$D_1 = Q_1 + T + Q_0 \cdot F$$

$$D_0 = F \cdot Q_0' + Q_0 \cdot F' + Q_1 \cdot F + Q_1 \cdot T$$

$$\text{Open} = Q_1 Q_0$$
 
## Vending Machine- D flip flops implementation



5p=F

10p=T

$$D_1 = Q_1 + T + Q_0 \cdot F$$

$$D_0 = F \cdot Q_0' + Q_0 \cdot F' + Q_1 \cdot F + Q_1 \cdot T$$

$$\text{Open} = Q_1 Q_0$$

## Vending Machine State Transition Diagram for J-K flip flops implementation

Present state		Inputs		Next state					
$Q_1$	$Q_0$	D	N	$D_1$	$D_0$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	0	0	0	X	0	X
		0	1	0	1	0	X	1	X
		1	0	1	0	1	X	0	X
		1	1	X	X	x	X	X	X
0	1	0	0	0	0	0	X	X	0
		0	1	1	0	1	X	X	1
		1	0	1	1	1	X	X	0
		1	1	X	X	x	X	X	X
1	0	0	0	1	0	x	0	0	X
		0	1	1	1	x	0	1	X
		1	0	1	1	x	0	1	X
		1	1	X	X	x	x	X	X
1	1	0	0	1	1	x	0	X	0
		0	1	1	1	x	0	X	0
		1	0	1	1	x	0	X	0
		1	1	X	X	x	x	X	X

# Vending Machine- K Maps for J-K flip flops implementation

**J<sub>1</sub>**

Q1Q0		Q1	
		11	10
DN	00	0	0
	01	0	1
	11	X	X
	10	1	1

Annotations: A vertical bracket on the right side of the table is labeled 'N'. A horizontal bracket at the bottom is labeled 'Q0'. A vertical bracket on the left side is labeled 'D'.

**K<sub>1</sub>**

Q1Q0		Q1	
		11	10
DN	00	x	x
	01	x	x
	11	X	X
	10	X	X

Annotations: A vertical bracket on the right side of the table is labeled 'N'. A horizontal bracket at the bottom is labeled 'Q0'. A vertical bracket on the left side is labeled 'D'.

**J<sub>0</sub>**

Q1Q0		Q1	
		11	10
DN	00	0	X
	01	1	X
	11	X	X
	10	0	X

Annotations: A vertical bracket on the right side of the table is labeled 'D'. A horizontal bracket at the bottom is labeled 'Q0'. A vertical bracket on the left side is labeled 'C'.

**K<sub>0</sub>**

Q1Q0		Q1	
		11	10
DN	00	X	0
	01	X	1
	11	X	X
	10	X	0

Annotations: A vertical bracket on the right side of the table is labeled 'N'. A horizontal bracket at the bottom is labeled 'B'. A vertical bracket on the left side is labeled 'D'.


**J<sub>1</sub> = ?**

**K<sub>1</sub> = ?**

**J<sub>0</sub> = ?**

**K = ?**
 
# Vending Machine- K Maps for J-K flip flops implementation




$$J_1 = D + Q_0 \cdot N$$

$$K_1 = 0$$

$$J_0 = Q_1' \cdot N + Q_1 \cdot D$$

$$K_0 = Q_1' \cdot N$$
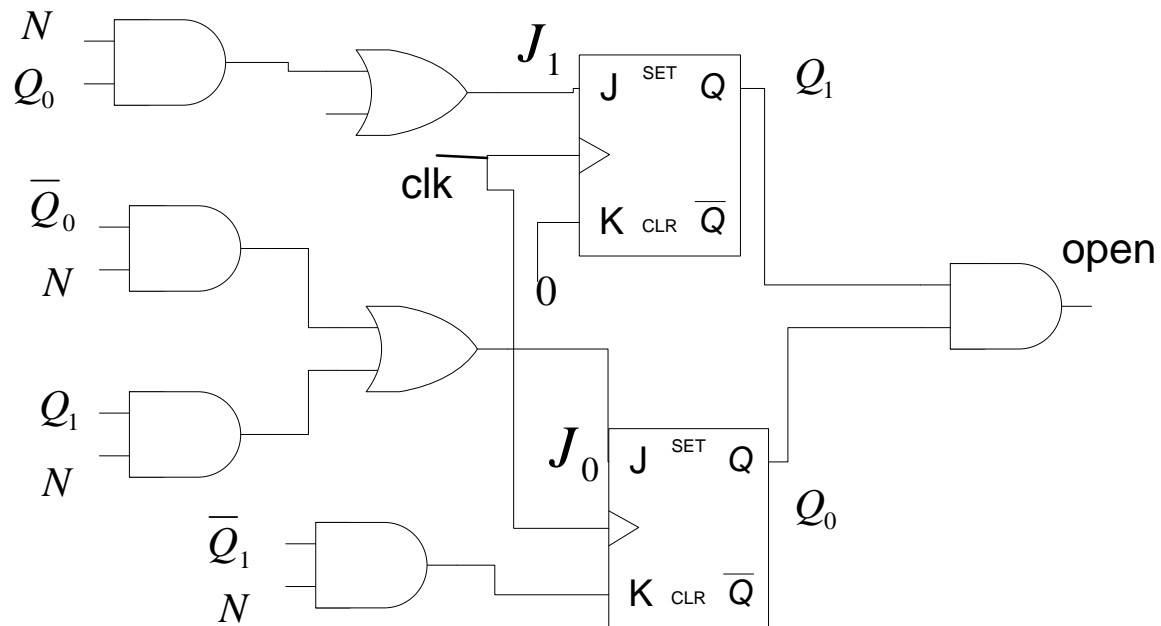
## Vending Machine- J-K flip flops implementation



$$J_1 = D + Q_0 \cdot N$$

$$J_0 = Q_1' \cdot N + Q_1 \cdot D$$

$$K_1 = 0$$

$$K_0 = Q_1' \cdot N$$

# Moore vs. Mealy FSM


- Design Moore and Mealy FSMs that detects

1101.




# State Transition Diagrams

Moore FSM

 

Mealy FSM: arcs indicate input/output

Mealy FSM

 

# Moore FSM State Transition Table

Current State			Inputs	Next State		
$S_2$	$S_1$	$S_0$	$A$	$S'_2$	$S'_1$	$S'_0$
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			

State	Encoding
S0	000
S1	001
S2	010
S3	011
S4	100

# Moore FSM State Transition Table

Current State			Inputs	Next State		
$S_2$	$S_1$	$S_0$	A	$S'_2$	$S'_1$	$S'_0$
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	0	1	0
0	1	1	0	0	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	0
1	0	0	1	0	1	0

State	Encoding
S0	000
S1	001
S2	010
S3	011
S4	100

# Moore FSM Output Table

Current State			Output
$S_2$	$S_1$	$S_0$	$Y$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	

# Moore FSM Output Table

Current State			Output
$S_2$	$S_1$	$S_0$	$Y$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1

$$Y = S_2$$

# Mealy FSM State Transition and Output Table

Current State		Input	Next State		Output
$S_1$	$S_0$	$A$	$S'_1$	$S'_0$	$Y$
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			


State	Encoding
S0	00
S1	01
S2	10
S3	11

# Mealy FSM State Transition and Output Table

Current State		Input	Next State		Output
$S_1$	$S_0$	$A$	$S'_1$	$S'_0$	$Y$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	1	0	1	1


State	Encoding
S0	00
S1	01
S2	10
S3	11

# Moore FSM Schematic

 




# Mealy FSM Schematic

 

# Moore and Mealy Timing Diagram

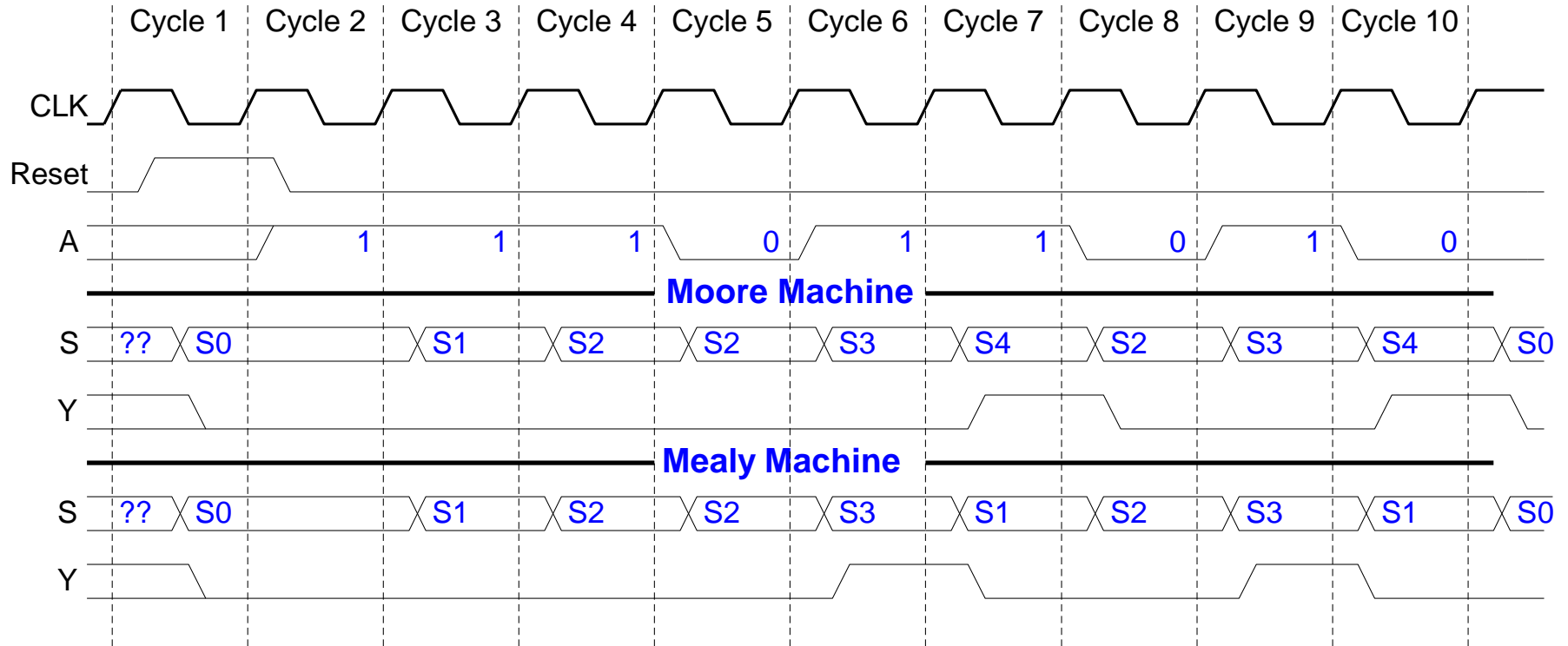


# Timing

- Flip-flop samples  $D$  at clock edge
- $D$  must be stable when it is sampled
- Similar to a photograph,  $D$  must be stable around the clock edge
- If  $D$  is changing when it is sampled, metastability can occur

 
# Input Timing Constraints

- Setup time:  $t_{\text{setup}}$  = time *before* the clock edge that data must be stable (i.e. not changing)
- Hold time:  $t_{\text{hold}}$  = time *after* the clock edge that data must be stable
- Aperture time:  $t_a$  = time around clock edge that data must be stable ( $t_a = t_{\text{setup}} + t_{\text{hold}}$ )


 
# Output Timing Constraints

- Propagation delay:  $t_{pcq}$  = time after clock edge that the output  $Q$  is guaranteed to be stable (i.e., to stop changing)
- Contamination delay:  $t_{ccq}$  = time after clock edge that  $Q$  might be unstable (i.e., start changing)




# Dynamic Discipline

- The input to a synchronous sequential circuit must be stable during the aperture (setup and hold) time around the clock edge.
- Specifically, the input must be stable
  - at least  $t_{\text{setup}}$  before the clock edge
  - at least until  $t_{\text{hold}}$  after the clock edge

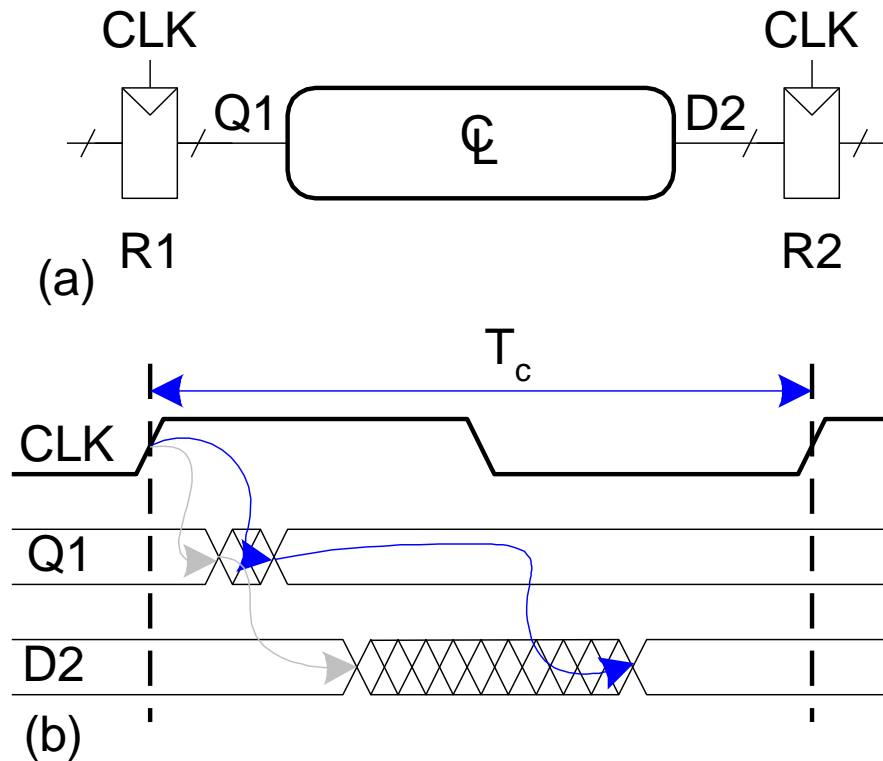
# Timing

- The delay between registers has a **minimum** and **maximum** delay, dependent on the delays of the circuit elements


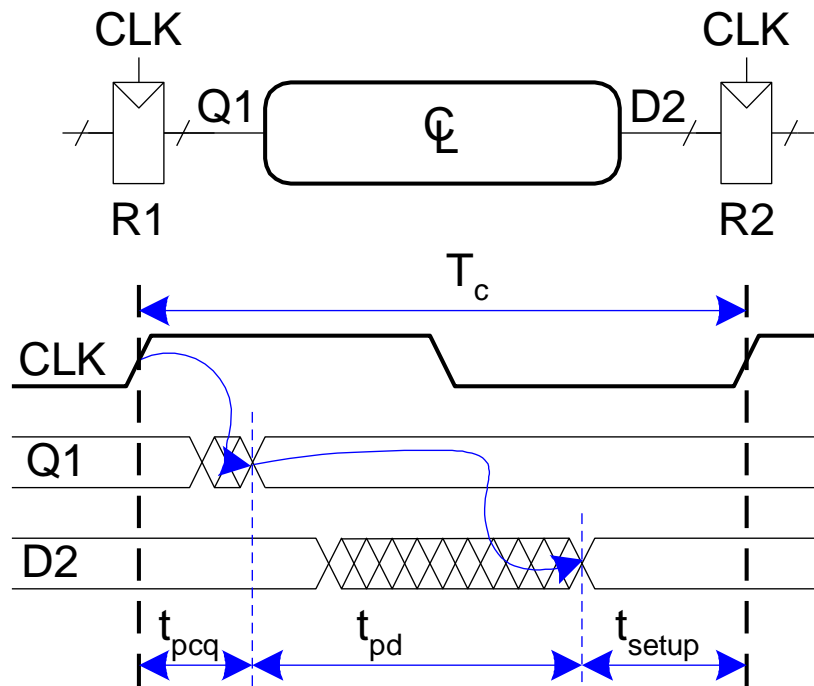
# Setup Time Constraint

- The setup time constraint depends on the **maximum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least  $t_{\text{setup}}$  before the clock edge.




$$T_c \geq$$


 
# Setup Time Constraint


- The setup time constraint depends on the **maximum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least  $t_{\text{setup}}$  before the clock edge.



$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$
$$t_{pd} \leq$$
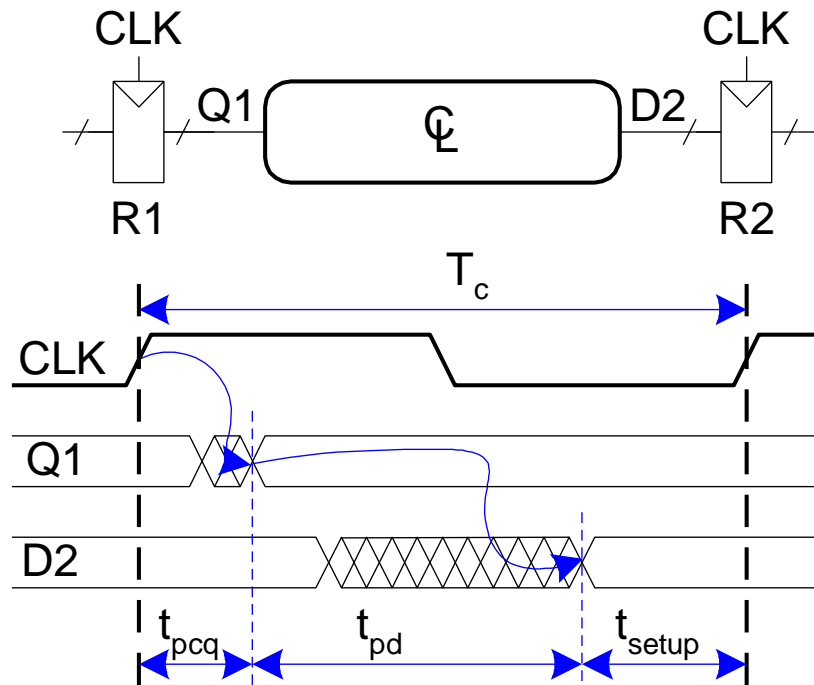
# Setup Time Constraint

- The setup time constraint depends on the **maximum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least  $t_{\text{setup}}$  before the clock edge.



$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{\text{setup}})$$