

INDIAN INSTITUTE OF TECHNOLOGY PATNA


CS226- Lab 8

Q1: Design a 2-bit counter that behaves according to the two control inputs I_0 and I_1 as follows. $I_0, I_1 = 0,0$: Stop counting; $I_0, I_1 = 0,1$: count up by one; $I_0, I_1 = 1,0$: count down by one; $I_0, I_1 = 1,1$: count by two. Implement using D,JK, RS and T flip flops. Show the design (hand written copy only)

(10+10+10+10=40 points)

Q2: Design a 4 bit asynchronous counter and test the output using a Seven segment display. Timing behavior is shown below. (10 points)

Timing Diagram:

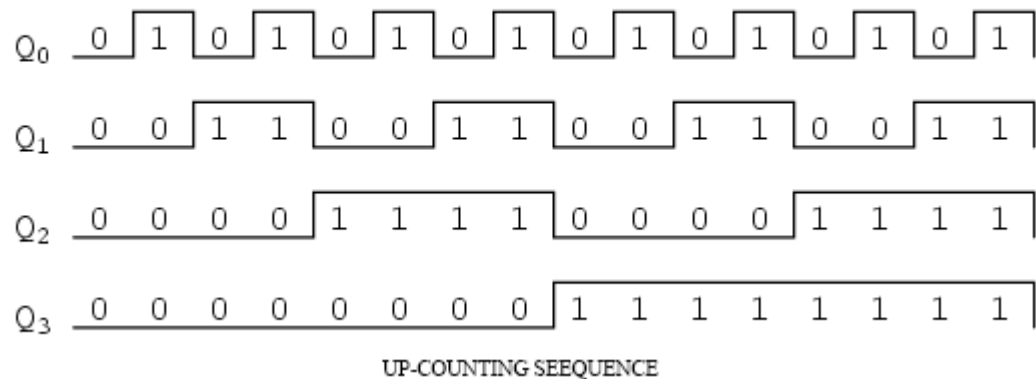

Q3: Design a 8 bit serial adder using Single full adder and registers.

Submission:

- ☐ Hand written design for Question 1 and **Simulation report** (screen shots of design and simulation output). The simulation files Q1.circ, Q1.circ, and Q2.circ,
- ☐ Zip the above files. file name is your role number.

Course work submission through:

<https://u.pcloud.com/#page=puplink&code=BRo7ZmzzIgDyLJP45iJdTOLbwQ70GwVeV>

This work is due 30th March 11.30 PM.