

REPORT


Que 1:-

I_1	I_0	Function
0	0	Stop Count
0	1	Count up by 1
1	0	Count down by 1
1	1	Count by 2

Count up
by 1

Count
down by
1

Count
by 2

 

Ans 2 :-

Comparison Between Two Designs

1) Without pipeline registers:

→ In this case we will get the output instantly i.e. after only 1 clock cycle. But the throughput of the design is less than that of the design with pipeline registers.


→ There is some delay due to the various gates used.

(ii) With pipeline registers.

In this case the delay will be same as that in the above case but the throughput will get doubled because of pipelining. We will get output after every two clock cycle ~~because~~ but throughput is doubled. Latency is same in both cases

Que 3:-

(i) For detecting odd.

 

S_1	S_0	A (Input)	S_1'	S_0'	Output (Y)
0	0	0	0	1	0
0	0	1	0	0	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	0	0	0
1	1	0	0	1	1
1	1	1	0	0	0


$S_0 S_1$	A	0	1
0 0		0 0	
0 1		0 0	
1 1		0 0	
1 0		1 0	

$$S_1' = \bar{S}_1 S_0 A + S_1 \bar{S}_0 \bar{A}$$

$$\bar{S}_0 = \bar{A}$$

$$Y = S_1 S_0 \bar{A}$$

(ii) For detecting 1001

 

S_1	S_0	Input (A)	S_1'	S_0'	Output (Y)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1

$S_1 S_0$	A	0	1
00		0	0
01		1	0
11		0	0
10		1	0


$S_1 S_0$	A	0	1
00		0	1
01		0	1
11		0	1
10		1	1

$$S_0' = S_1 \bar{S}_0 + A$$

$$S_1' = \bar{S}_1 S_0 \bar{A} + S_1 \bar{S}_0 \bar{A}$$

$$Y = S_1 S_0 A$$

(iii) For detecting 1011

 

s_1	s_0	Input (A)	s_1'	s_0'	Output (Y)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	0	1	1

$s_1 s_0$		A	
		0	1
0 0		0	0
0 1		1	0
1 1		1	0
0 0		0	1

$s_1 s_0$		A	
		0	1
0 0		0	1
0 1		0	1
1 1		0	1
1 0		0	1

$$s_1' = s_1 \bar{s}_0 A + s_0 \bar{A}$$

$$s_0' = A$$

$$Y = s_1 s_0 A$$

→ For detecting either of 0100, 1001 and 1011, we will simply take OR of these three cases.