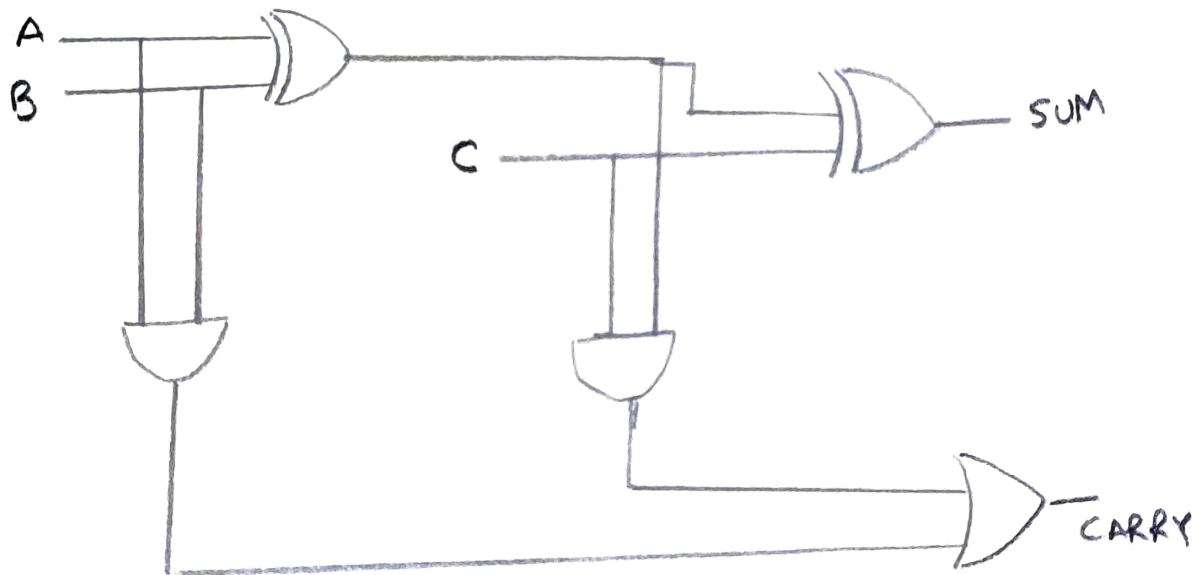



# CS-322

## 1 - Bit Full Adder



A, B  $\rightarrow$  2 Inputs

C  $\rightarrow$  CARRY-IN

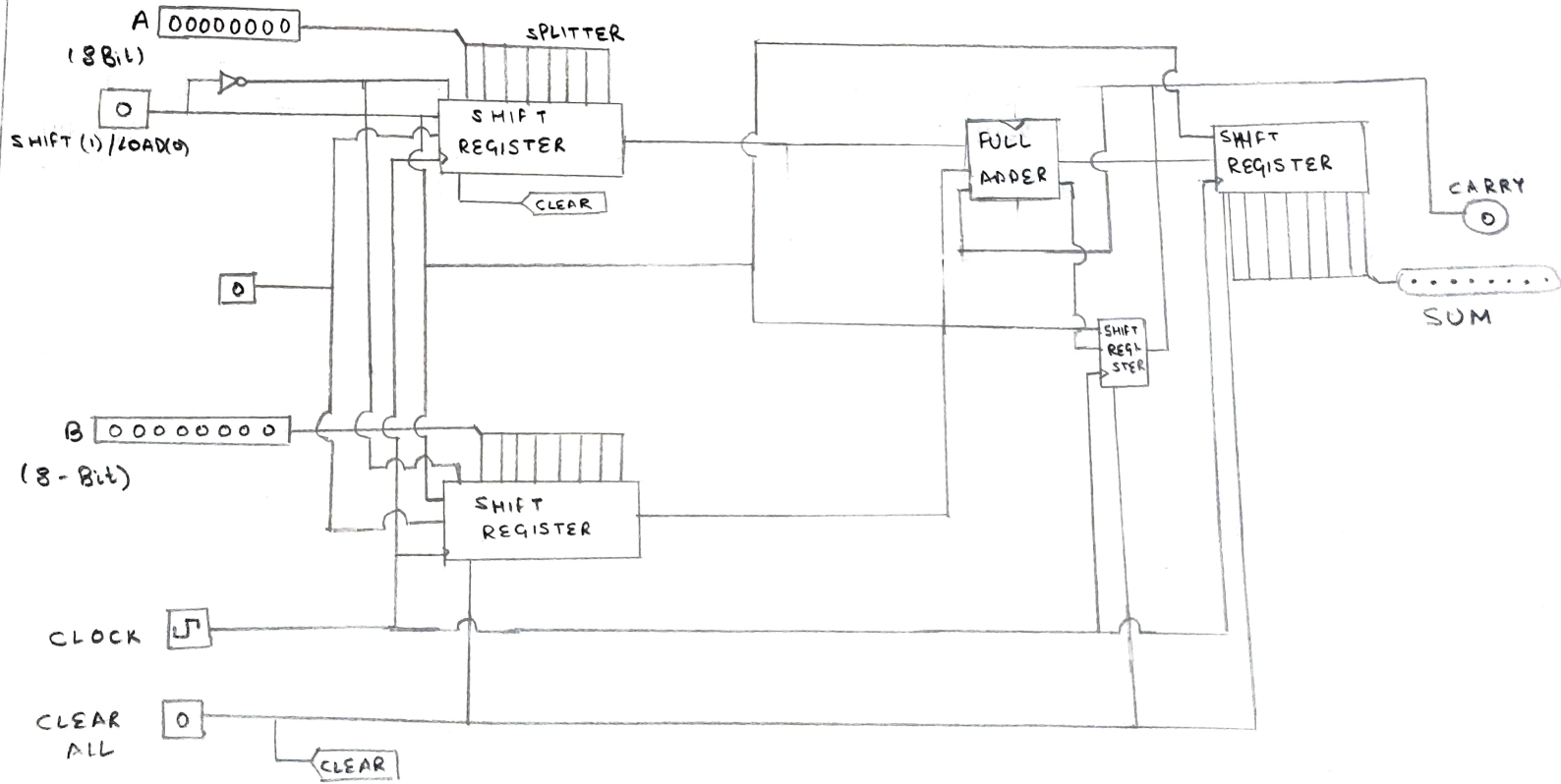

8 Bit Serial Adder Using A Single Full Adder