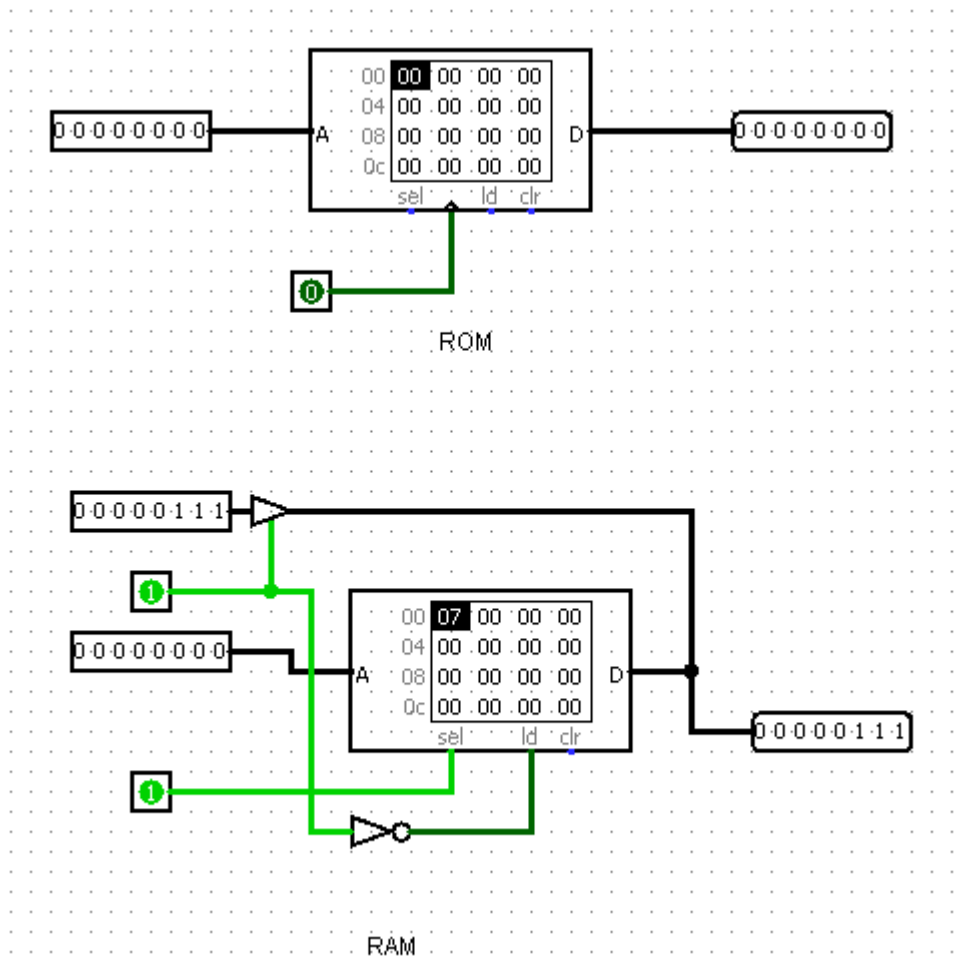


Q1: Simulate the following RAM and ROM modules using logic-sim. Simulate for various ROM/RAM sizes.


(10 points)



Q2: Design and simulate a $2M \times 32$ memory system using $512K \times 8$ memory blocks?

(15 points)

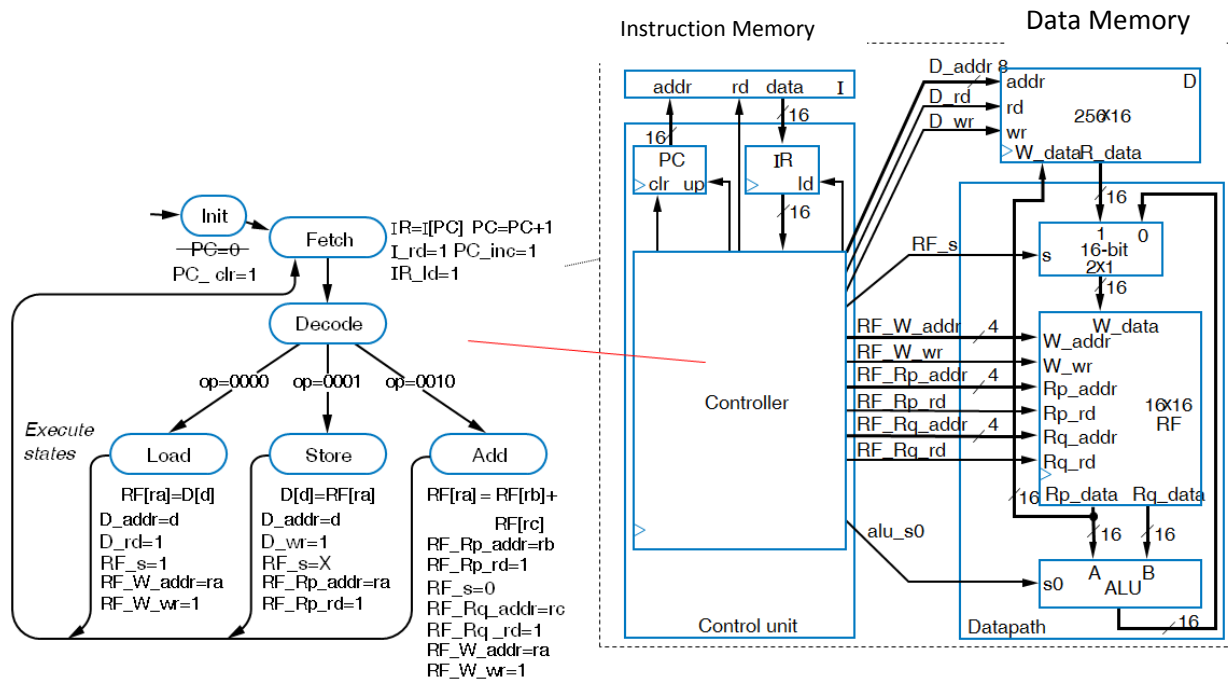Q3: Design and simulate architecture shown below (combines ALU, Memory and FSM). Write a simple program to add two numbers and store the result in another memory location. Details in the ppt.



(75 points)

Submit your .circ file containing your implementations

<https://u.pcloud.com/#page=puplink&code=9nykZk5X2GpdktxJw4HjC7KDAS4unmP3X>

This work is due on: : 18th April 11.30 PM