

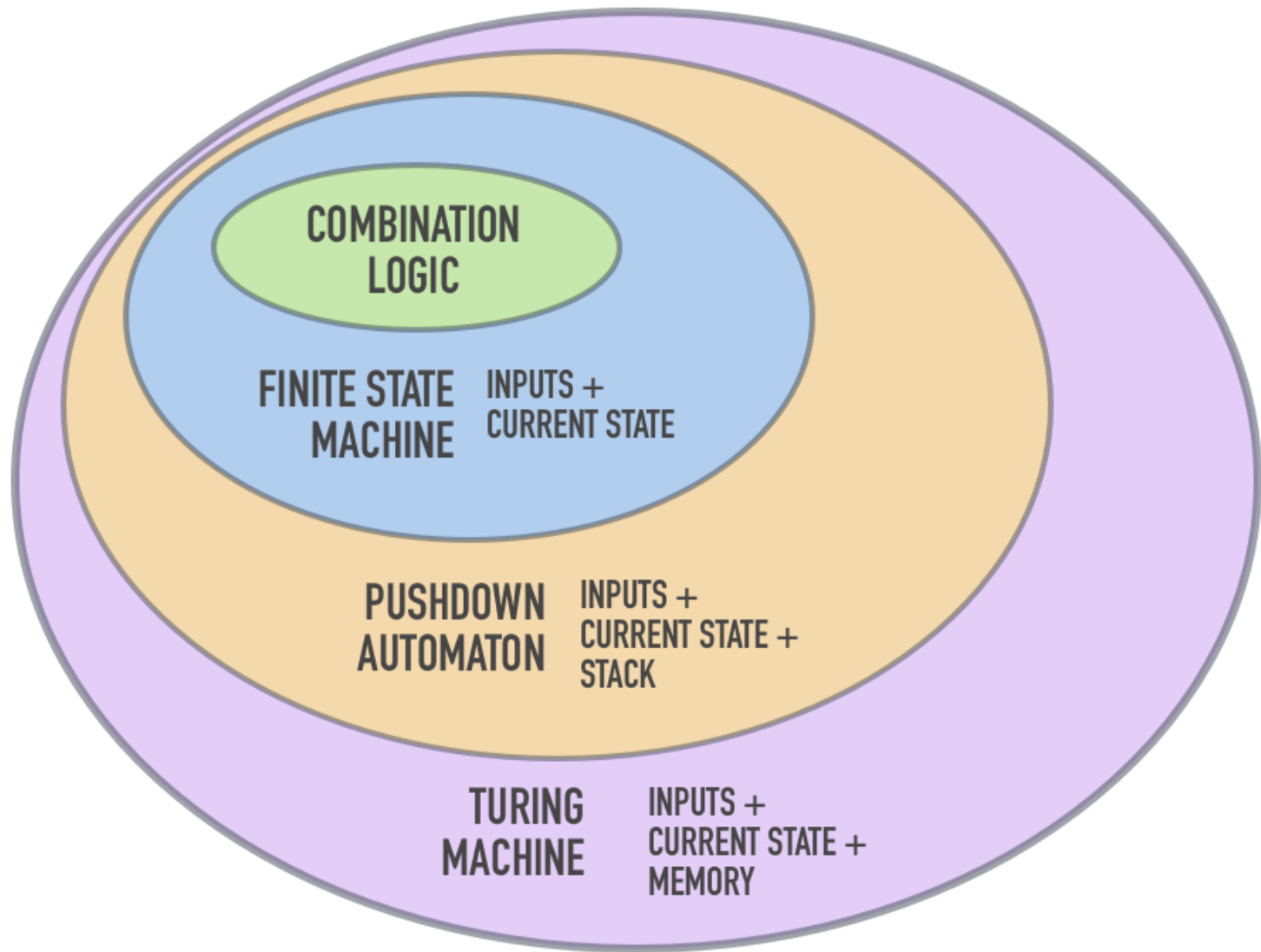

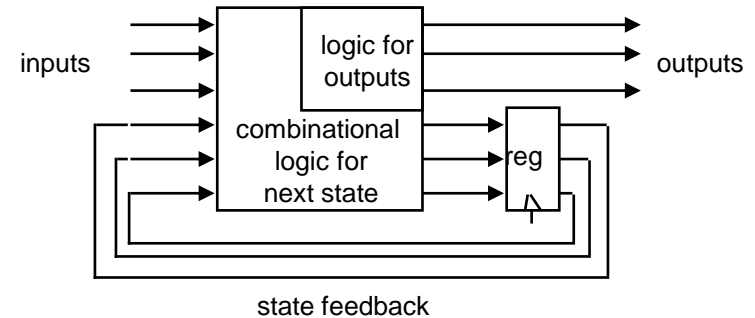
# **Finite-State Machines** **(FSMs) and Controllers**



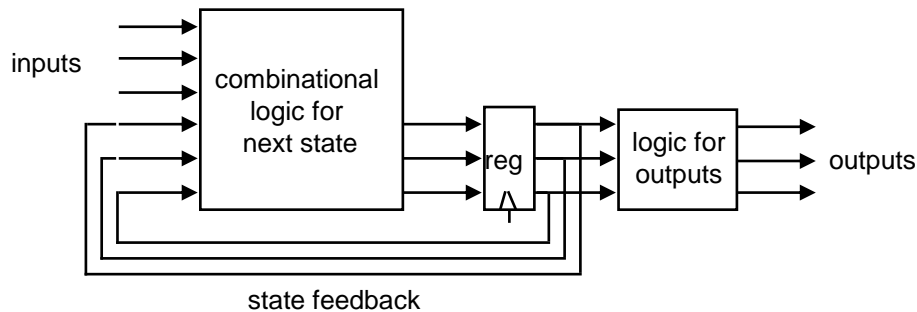
# Mealy and Moore machines

- Mealy machines tend to have fewer states
- Mealy machines react faster to inputs
- Moore machines are generally safer to use
  - outputs change at clock edge (always one cycle later)
  - in Mealy machines, input change can cause output change as soon as logic is done



# Mealy and Moore machines

 


Moore (a) and Mealy (b)

State : SR, D, T, J-K, memory


 
# Finite state machine representations

- States: determined by possible values in sequential storage elements
- Transitions: change of state
- Clock: controls when state can change by controlling storage elements
- Sequential logic
  - sequences through a series of states
  - based on sequence of values on input signals
  - clock period defines elements of sequence



  
# sequential system- represented with a state diagram

- Shift register
  - input value shown on transition arcs
  - output values shown within state node


 
# Counters are simple finite state machines

- Counters
  - proceed through well-defined sequence of states in response to enable
- Many types of counters: binary, BCD, Gray-code
  - 3-bit up-counter: 000, 001, 010, 011, 100, 101, 110, 111, 000, ...
  - 3-bit down-counter: 111, 110, 101, 100, 011, 010, 001, 000, 111, ...




# How do we turn a state diagram into logic?

- Counter
  - 3 flip-flops to hold state
  - logic to compute next state
  - clock signal controls when flip-flop memory can change
    - wait long enough for combinational logic to compute new value
    - don't wait too long as that is low performance


 
# How do we turn a state diagram into logic?



Q	Q(next)	D
0	0	0
0	1	1
1	0	0
1	1	1

Present state    Next state

Flip flop input

C3	C2	C1	N3	N2	N1	D3	D2	D1
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0

$$D1 = C1'$$

$$D2 = C1C2' + C1'C2$$




$$= C1 \text{ xor } C2$$

$$D3 = C1C2C3' + C1'C3 + C2'C3$$

$$= (C1C2)C3' + (C1' + C2')C3$$


$$= (C1C2)C3' + (C1C2)'C3$$

$$= (C1C2) \text{ xor } C3$$

   
 
# How do we turn a state diagram into logic? (3 bit counter)

- Counter
  - 3 flip-flops to hold state
  - logic to compute next state
  - clock signal controls when flip-flop memory can change
    - wait long enough for combinational logic to compute new value
    - don't wait too long as that is low performance





# How do we turn a state diagram into logic? (using J-K)

Present state    Next state


Flip flop input

C3	C2	C1	N3	N2	N1	J3	K3	J2	K2	J1	K1
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

Q	Q(next)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

  

$$J3 = C1C2$$


 


$$K3 = C1C2$$

# How do we turn a state diagram into logic? (using J-K)

Present state    Next state    Flip flop input

C3	C2	C1	N3	N2	N1	J3	K3	J2	K2	J1	K1
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

  


# How do we turn a state diagram into logic? (using J-K)


Present state    Next state

Flip flop input

C3	C2	C1	N3	N2	N1	J3	K3	J2	K2	J1	K1
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

 

J1=1

 

K1=1

# How do we turn a state diagram into logic? (using J-K)

Present state    Next state

Flip flop input

C3	C2	C1	N3	N2	N1	J3	K3	J2	K2	J1	K1
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

$$J3 = C1C2$$


$$K3 = C1C2$$

$$J2 = C1$$


$$K2 = C1$$

$$J1 = 1$$

$$K1 = 1$$

 
 
# How do we turn a state diagram into logic? (Using T-FF)






Q	Q(next)	T
0	0	0
0	1	1
1	0	1
1	1	0

Present state    Next state

Flip flop input

C3	C2	C1	N3	N2	N1	T3	T2	T1
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

   
$$\begin{aligned} T1 &= 1 \\ T2 &= C1 \\ T3 &= C2C1 \end{aligned}$$




# How do we turn a state diagram into logic? (Using SR-FF)

Present state    Next state    Flip flop input


C3	C2	C1	N3	N2	N1	S3	R3	S2	R2	S1	R1
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	0	0	X	1	0	0	1
0	1	0	0	1	1	0	X	X	0	1	0
0	1	1	1	0	0	1	0	0	1	0	1
1	0	0	1	0	1	X	0	0	X	1	0
1	0	1	1	1	0	X	0	1	0	0	1
1	1	0	1	1	1	X	0	X	0	1	0
1	1	1	0	0	0	0	1	0	1	0	1

 

Q	Q(next)	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

 

$$S1 = C1'$$

 


$$R1 = C1$$



# How do we turn a state diagram into logic? (Using S-R FF)

Present state    Next state    Flip flop input

C3	C2	C1	N3	N2	N1	S3	R3	S2	R2	S1	R1
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	0	0	X	1	0	0	1
0	1	0	0	1	1	0	X	X	0	1	0
0	1	1	1	0	0	1	0	0	1	0	1
1	0	0	1	0	1	X	0	0	X	1	0
1	0	1	1	1	0	X	0	1	0	0	1
1	1	0	1	1	1	X	0	X	0	1	0
1	1	1	0	0	0	0	1	0	1	0	1

 

Q	Q(next)	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

C3C2

C1

	C3	C2	C1
C3	0	X	X
C2	1	0	0
C1	0	1	1

$$S2 = C1C2'$$

C3

C1


	C3	C2	C1
C3	X	0	0
C2	0	1	1
C1	X	0	0

$$R2 = C1C2$$

# How do we turn a state diagram into logic? (Using S-R FF)

Present state    Next state    Flip flop input

C3	C2	C1	N3	N2	N1	S3	R3	S2	R2	S1	R1
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	0	0	X	1	0	0	1
0	1	0	0	1	1	0	X	X	0	1	0
0	1	1	1	0	0	1	0	0	1	0	1
1	0	0	1	0	1	X	0	0	X	1	0
1	0	1	1	1	0	X	0	1	0	0	1
1	1	0	1	1	1	X	0	X	0	1	0
1	1	1	0	0	0	0	1	0	1	0	1

 

Q	Q(next)	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

C1 \ C3C2

	C3	C2	
C1	0	0	X
C1	0	1	0
	C2		

$$S3 = C1C2C3'$$

C1 \ C3


	C3	
C1	X	0
C1	X	1
	C2	

$$R3 = C1C2C3$$


# shift register

Present state      Next state

In	C1	C2	C3	N1	N2	N3
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	0	1
1	0	1	1	1	0	1
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	1	1	1
1	1	1	1	1	1	1

 

D1 = In  
D2 = C1  
D3 = C2

 

Do as an exercise: flip flop inputs table, logic (D1, D2, D3) and Simplification