

# CS 225: Switching Theory

S. Tripathy  
IIT Patna

# Previous Class

Switching Algebra

# This Class

- Switching Algebra
- - Switching circuit
  - Propositional calculus

# Functional Properties

---

Let binary constant  $a_i$  be the value of function  $f(x_1, x_2, \dots, x_n)$  for the combination of variables whose decimal code is  $i$ . Thus,

$$f(x_1, x_2, \dots, x_n) = a_0 x_1' x_2' \dots x_n' + a_1 x_1' x_2' \dots x_n + \dots + a_r x_1 x_2 \dots x_n$$

The coefficient  $a_i$  is set to 1 (0) if the corresponding minterm is (is not) in the canonical form

Since there are  $2^n$  coefficients, each of which can have two values, 0 and 1, there are  $2^{2^n}$  possible switching functions of  $n$  variables

Example: Canonical sum-of-products form for two variables

$$f(x, y) = a_0 x' y' + a_1 x' y + a_2 x y' + a_3 x y$$

Thus  $2^{2^2} = 16$  functions corresponding to the 16 possible assignments of 0's and 1's to  $a_0, a_1, a_2$ , and  $a_3$

# List of Functions of Two Variables

a3	a2	a1	a0	f(x,y)	Name of Function	Symbol
0	0	0	0	0	Inconsistency	
0	0	0	1	$x'y'$	NOR	$x \downarrow y$
0	0	1	0	$x'y$	NOT	$x'$
0	0	1	1	$x'$		
0	1	0	0	$xy'$		
0	1	0	1	$y'$		
0	1	1	0	$x'y+xy'$	Exclusive OR	$x \oplus y$
0	1	1	1	$x'+y'$	NAND	$x   y$

a3	a2	a1	a0	f(x,y)	Name of Function	Symbol
1	0	0	0	$xy$	AND	$x.y$
1	0	0	1	$xy+x'y'$	Equivalence	$x \equiv y$
1	0	1	0	$y$		
1	0	1	1	$x'+y$	Implication	$x \rightarrow y$
1	1	0	0	$x$		
1	1	0	1	$x+y'$	Implication	$y \rightarrow x$
1	1	1	0	$x+y$	OR	$x + y$
1	1	1	1	1	Tautology	

# Functionally Complete Operations

---

Every switching function can be expressed in canonical form consisting of a finite number of switching variables, constants and operations  $+$ ,  $.$ ,  $'$

A set of operations is functionally complete (or universal) if and only if every switching function can be expressed by operations from this set

Example: Set  $\{+, ., '\}$

Set  $\{+, '\}$ ?

Yes, since using De Morgan's theorem,  $x . y = (x' + y)'$ .

Thus,  $+$  and  $'$  can replace the  $.$  in any switching function

Set  $\{., '\}$

Yes for similar reasons

NAND:?

Yes,  $\text{NAND}(x,x) = x'$  and  $\text{NAND}[\text{NAND}(x,y), \text{NAND}(x,y)] = xy$

NOR:?

Yes,  $\text{NOR}(x,x) = x'$  and  $\text{NOR}[\text{NOR}(x,y), \text{NOR}(x,y)] = x + y$

# Isomorphic Systems

---

Isomorphism: Two algebraic systems are isomorphic if

- For every operation in one system, there exists a corresponding operation in the second system
- To each element  $x_i$  in one system, there corresponds a unique element  $y_i$  in the other system, and vice versa
- If each operation and element in every postulate of one system is replaced by the corresponding operation and element in the other system, then the resulting postulate is valid in the second system

Thus, two algebraic systems are isomorphic if and only if they are identical except the labels and symbols used to represent the operations and elements

# Transmission Function

---

**Transmission function for a circuit:** assumes value 1 (0) when there is (there is not) a path from one terminal of the circuit to the other through which information flows

Definition of transmission functions

x	y	$x + y$	$xy$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

**Analogy:** OR  $\leftrightarrow$  parallel; AND  $\leftrightarrow$  series

Complement of a given circuit: one that blocks all paths of information flow whenever the given circuit permits any

Thus, **algebraic system for switching circuits isomorphic to switching algebra**



# Propositional Calculus

---

**Proposition:** declarative statement which may be either true or false

**Example:** temperature is 100 degree Celsius  
turtle runs faster than the hare  
sum of 2 and 3 equals 5

**Proposition variable:** 1 (0) if proposition is true (false)

**Negation  $p'$  of proposition  $p$ :** 1 (0) if  $p$  is 0 (1)

**Conjunction of propositions  $p$  and  $q$  is  $pq$ :** true when both  $p$  and  $q$  are true and false whenever either one or both  $p$  and  $q$  are false

**Disjunction of propositions  $p$  and  $q$  is  $p + q$ :** true when either  $p$  or  $q$  or both are true and false whenever both  $p$  and  $q$  are false

# Propositional Calculus (Contd.)

---

Definition of conjunction and disjunction of  $p$  and  $q$

$p$	$q$	$pq$	$p + q$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

- **Analogy:** OR  $\leftrightarrow$  disjunction; AND  $\leftrightarrow$  conjunction
- Thus, algebraic system for switching circuits is isomorphic to propositional calculus

# Propositional Calculus Example

---

**Example:** Air-conditioning of a storage warehouse to be turned on if one or more of the following three conditions occurs:

1. Weight of stored material is less than 100 kg, relative humidity is at least 60%, and temperature is above 60 degrees Celsius
2. Weight of stored material is 100 kg or more and temperature is above 60 degrees Celsius
3. Weight of the stored material is less than 100 kg and the barometer stands at 30 inches of mercury or over

# Propositional Calculus Example (Contd.)

---

A: proposition that air-conditioning is turned on

W: weight of 100 kg or more

H: relative humidity of at least 60%

T: temperature above 60 degrees Celsius

P: barometric pressure is 30 inches of mercury or more

$$A = W'HT + WT + W'P$$

$$= HT + WT + W'P$$

$$= T(H+W) + W'P$$

Thus, air-conditioning is on if the temperature is above 60 degrees Celsius and either the weight is at least 100 kg or the humidity is at least 60%, or if the weight is less than 100 kg and the barometer stands at 30 inches or over

# Electronic Gate Networks

---

**Electronic gates:** generally receive voltages as inputs and produce output voltages

**Precise values of voltages not significant:** restricted to value ranges - high (value 1) and low (value 0)


**Electronic gates constructed with two-state switching devices:** each capable of permitting the flow of current or blocking it

**To implement arbitrary switching functions:** gates must be able to implement a functionally complete set of operations


## Functionally Complete Set



(a) AND gate.

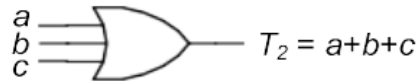


(b) OR gate.

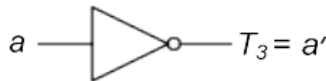

(c) NOT gate.
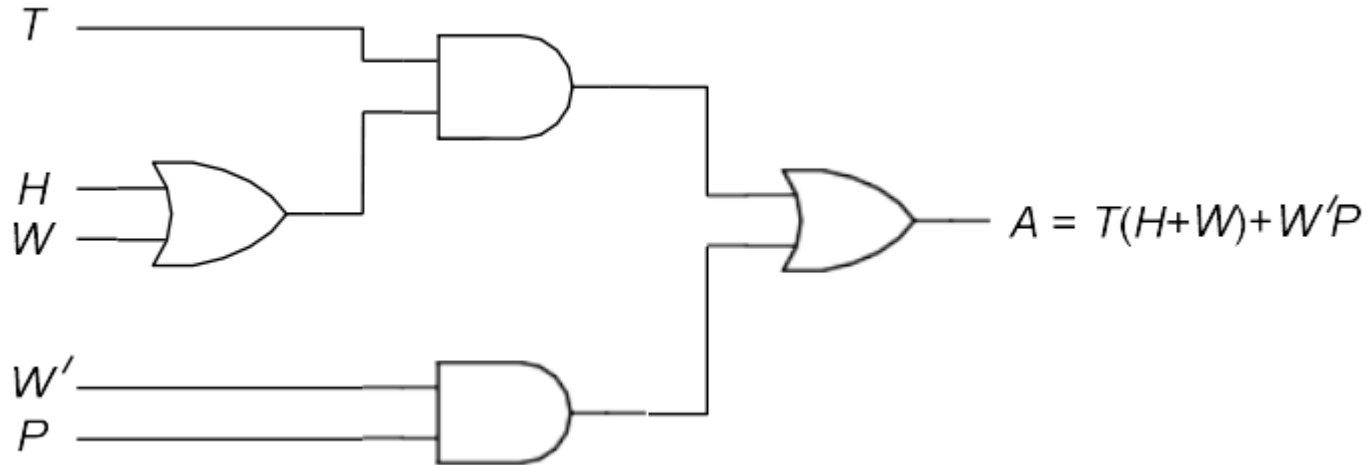
## Gate Network for Air-conditioning Function



# Boolean Algebra

---

**Boolean algebra B:** A set of elements  $a, b, c, \dots$ , and binary operations  $+$  and  $\cdot$  that satisfy the idempotent, commutative, absorption, and associative laws, and are mutually distributive

Complement  $a'$  of any element  $a$  in  $B$  is unique, i.e., there exists only element  $a'$  such that  $a + a' = 1$  and  $a \cdot a' = 0$

- Suppose there exists element  $a$  which has two complements,  $b_1$  and  $b_2$ ,  
i.e.,  $a + b_1 = 1$ ,  $a \cdot b_1 = 0$ ,  $a + b_2 = 1$ ,  $a \cdot b_2 = 0$ 
  - Then  $b_1 = b_1 \cdot 1 = b_1 \cdot (a + b_2) = b_1 \cdot a + b_1 \cdot b_2 = 0 + b_1 \cdot b_2 = b_1 \cdot b_2$
- Similar arguments show  $b_2 = b_1 \cdot b_2$ .
- Thus,  $b_1 = b_2$ , proving the uniqueness of the complement

**Complements of elements 0 and 1:** since by definition  $0 + 0' = 1$ ,  $0' = 1$ . Similarly,  $1' = 0$

# De Morgan's Theorem

---

Prove De Morgan's theorem for two variables:

$$(a + b)' = a' \cdot b'$$

$$(a \cdot b)' = a' + b'$$

- We have to show that  $(a + b)(a' \cdot b') = 0$  and  $(a + b) + a' \cdot b' = 1$
- Applying the distributive law:
  - $(a + b) + a'b' = (a + b + a')(a + b + b') = (b + 1)(a + 1) = 1$
- Dual property proved similarly

Definition of a Boolean algebra isomorphic to switching algebra

+	0   1	.	0   1	
0	0   1	0	0   0	$0' = 1$
1	1   1	1	0   1	$1' = 0$



# De Morgan's Theorem

---

Example of Boolean algebra:

+	0 1 a b	.	0 1 a b	
0	0 1 a b	0	0 0 0 0	$0' = 1$
1	1 1 1 1	1	0 1 a b	$1' = 0$
a	a 1 a 1	a	0 a a 0	$a' = b$
b	b 1 1 b	b	0 b 0 b	$b' = a$

# Boolean Algebra Operator Precedence

- Evaluate the following Boolean equations, assuming  $a=1$ ,  $b=1$ ,  $c=0$ ,  $d=1$ .

- Q2.  $F = ab + c$ .

- Answer: first  $*$  ( . AND) So on.

- Q3.  $F = ab'$ .

- Answer: we first evaluate  $b'$  because NOT has precedence over AND, resulting in  $F = 1 * (1') = 1 * (0) = 1 * 0 = 0$ .

*a*

Boolean algebra precedence, highest precedence first.

Symbol	Name	Description
( ) first	Parentheses	Evaluate expressions nested in parentheses
'	NOT	Evaluate from left to right
*	AND	Evaluate from left to right
+	OR	Evaluate from left to right

- Thanks
- Q2 on Next Week